

Name of the college: Sadguru Gadage Maharaj college, KaradSubject: Electronics

Expt. No. 6

Name: [REDACTED]

Class: BCS-I Batch: [REDACTED]

Roll No.: [REDACTED]

Date 28/8/24Title of Expt.: Full Adder

Aim - To study of the Full Adder

Equipment - Ic 7486, 7408, 7432, power supply etc

Logic Diagram -

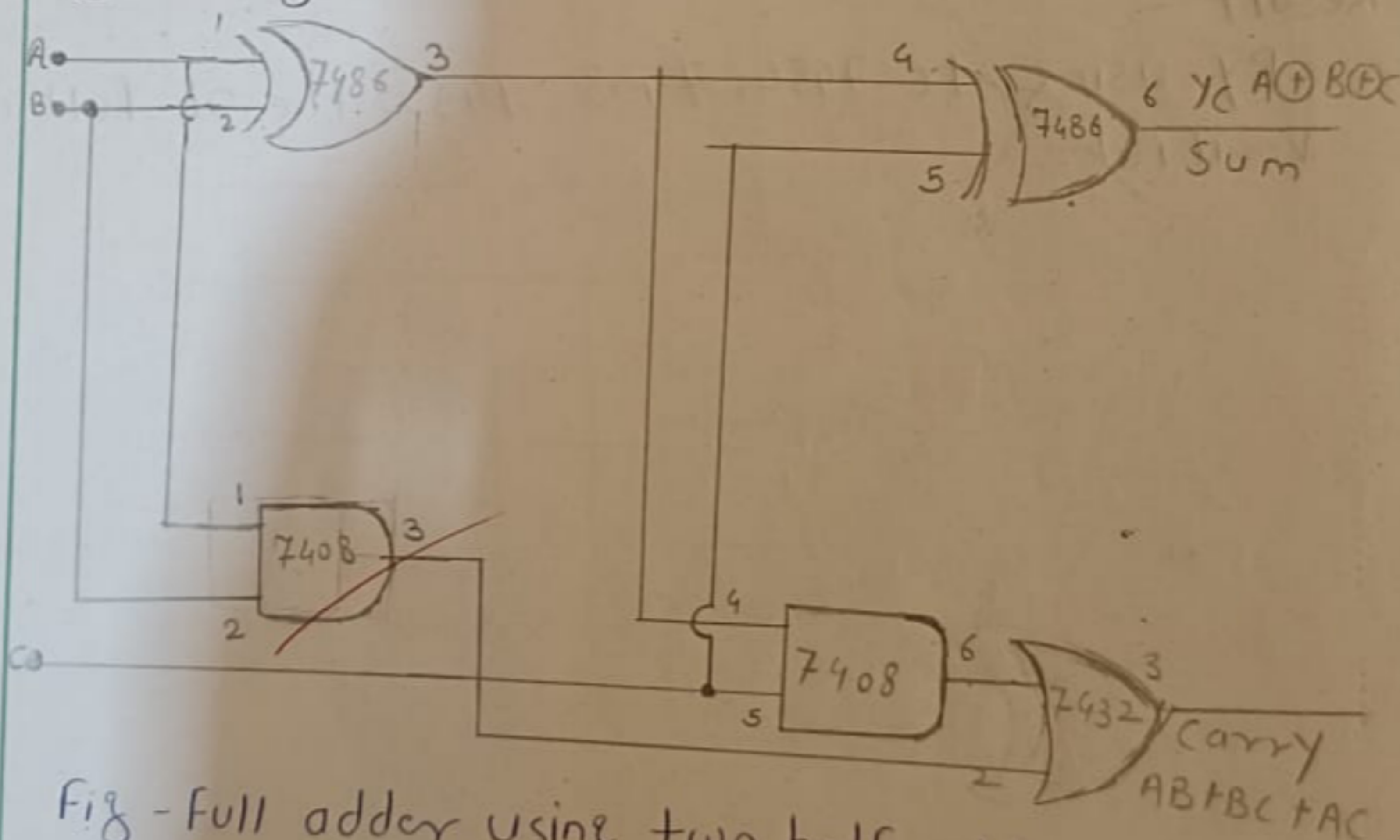


Fig - Full adder using two half adder

Remarks

Shot on OnePlus

By sakshi

Truth Table -

Input			Output	
A	B	C	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Result -

By using IC 7486, 7408, 7432 the OF Full adder is verified.