



Name of the college: Sadguru Gadage Maharaj college, Karad
Subject: Electronics

Expt. No. 5

Name: [REDACTED]

Class: Bcs-I Batch: [REDACTED]


Roll No.: [REDACTED]

Date 9/10/29Title of Expt.: OP-amp as adder


Aim - To study the application of OP-AMP as adder.

Apparatus - OP-amp 741, resistor, dual Power supply

circuit diagram -

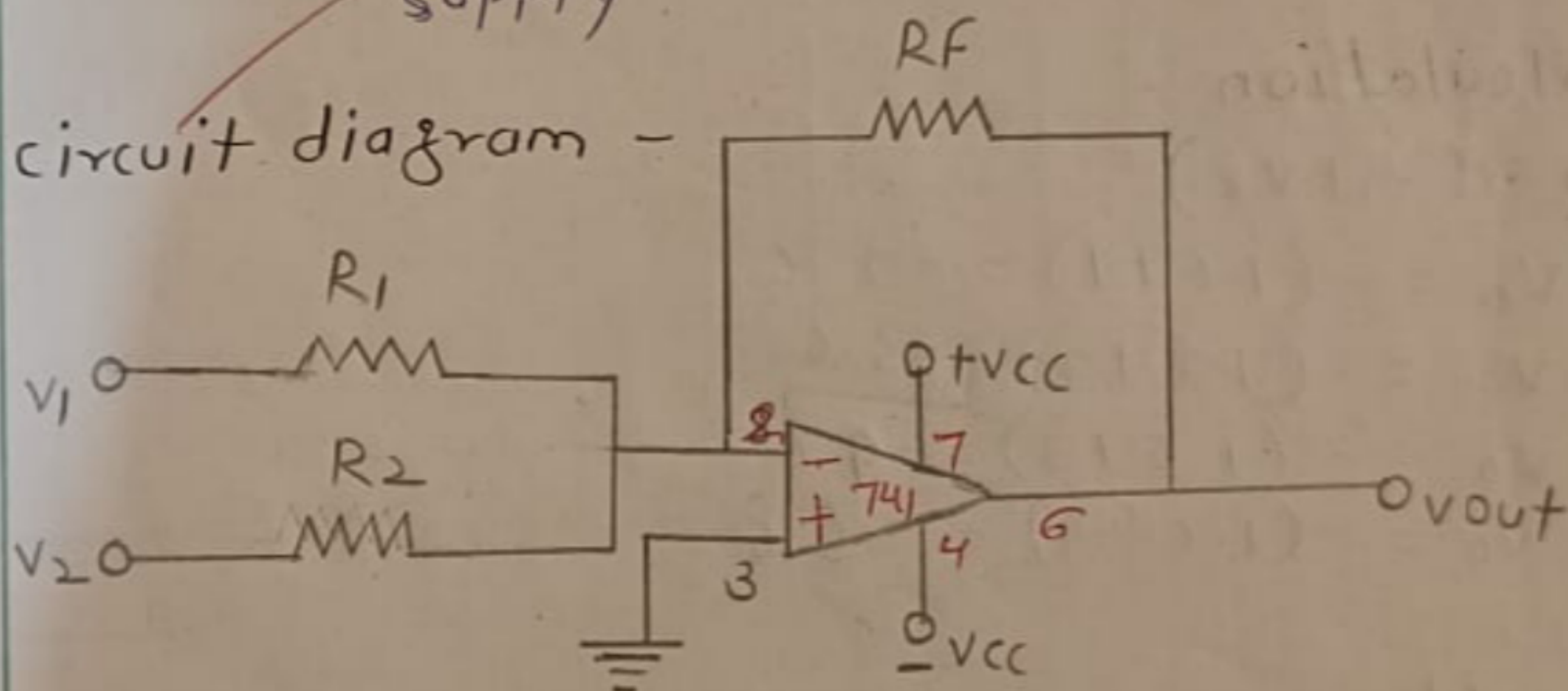

Pic Diagram -

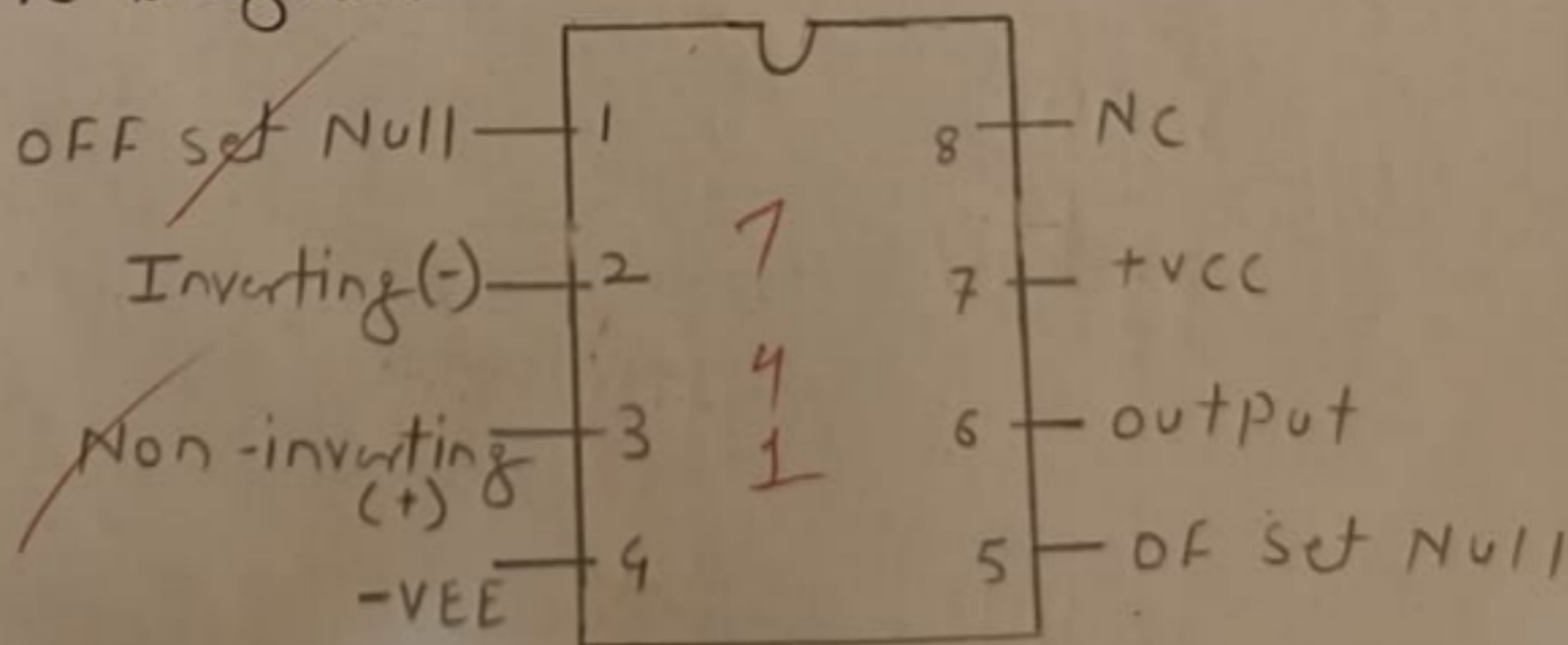

Remarks

Signature
9-10-2024
Signature

Observation Table -

Obs No	V_1	V_2	Output Voltage $V_o = (V_1 + V_2)$	
			calculated	observed
1.	1.6	1	2.6	-2.61
2.	1.6	2	3.6	-3.67
3.	1.6	3	4.6	-4.58
4.	1.6	4	5.6	-5.70

Calculation -

$$V_o = (V_1 + V_2)$$

$$1] V_o = -(1.6 + 1) = -2.6$$

$$2] V_o = -(1.6 + 2) = -3.6$$

$$3] V_o = -(1.6 + 3) = -4.6$$

$$4] V_o = -(1.6 + 4) = -5.6$$

Result -

Studied op-AMP as adder circuit